

Name: \_\_\_\_\_

Lab Partners: \_\_\_\_\_

Mini Lab 2.1

1) Draw a circuit diagram of a circuit with two batteries wired in **series** and two lightbulbs wired in **series**.

2) Build this circuit and make observations about brightness and what would happen if a bulb went out.

---

---

---

3) Voltage across 1<sup>st</sup> light bulb. Prediction, (with explanation): \_\_\_\_\_

---

---

Measurement: \_\_\_\_\_

4) Voltage across 2<sup>nd</sup> light bulb. Prediction, (with explanation): \_\_\_\_\_

---

---

Measurement: \_\_\_\_\_

4) Voltage across both light bulbs. Prediction, (with explanation): \_\_\_\_\_

---

---

Measurement: \_\_\_\_\_

5) Current through circuit. Prediction, (with explanation): \_\_\_\_\_

---

---

Measurement: \_\_\_\_\_

Mini Lab 2.2

1) Draw a circuit diagram of a circuit with two batteries wired in **series** and two lightbulbs wired in **parallel**.

2) Build this circuit and make observations about brightness and what would happen if a bulb went out.

---

---

---

3) Voltage across 1<sup>st</sup> light bulb. Prediction, (with explanation): \_\_\_\_\_

---

---

Measurement: \_\_\_\_\_

4) Voltage across 2<sup>nd</sup> light bulb. Prediction, (with explanation): \_\_\_\_\_

---

---

Measurement: \_\_\_\_\_

5) Current through 1<sup>st</sup> loop. Prediction, (with explanation): \_\_\_\_\_

---

---

Measurement: \_\_\_\_\_

5) Current through 2<sup>nd</sup> loop. Prediction, (with explanation): \_\_\_\_\_

---

---

Measurement: \_\_\_\_\_