

Ohm's Law PS

1. $I = 1.00 \text{ mA} = 1 \times 10^{-3} \text{ A} = .001 \text{ A}$
 $t = 60.0 \text{ s}$

a) $I = \frac{q}{t}$ $(.001 = \frac{q}{60}) 60$ $q = 0.06 \text{ C}$

b) 0.06 C $| e = 1.6 \times 10^{-19} \text{ C}$

$$0.06 \text{ C} \left(\frac{1 \text{ electron}}{1.6 \times 10^{-19} \text{ C}} \right) = 3.75 \times 10^{17} \text{ electrons}$$

c) 0 protons (they don't move)

2. $R = 1 \times 10^4 \Omega = 10,000$
 $I = 30.0 \text{ mA} = 30 \times 10^{-3} \text{ A} = 0.0300 \text{ A}$
 $V = ?$

$$V = IR$$

$$V = (10,000)(.3) = 3000 \text{ V} = 3.00 \times 10^3 \text{ V}$$

to show 3 sig figs
we need to use
scientific notation

3. $R = 1.25 \text{ k}\Omega = 1.25 \times 10^3 \Omega = 1250 \Omega$
 $I = 1.03 \text{ mA} = 1.03 \times 10^{-3} \text{ A} = 0.00103 \text{ A}$
 $V = ?$ (potential difference is voltage)

$$V = IR$$

$$V = (0.00103)(1250) = 1.29 \text{ V}$$

4. The configuration with 1 $10\text{-}\Omega$ resistor, because it has less total resistance than the 3 $5\text{-}\Omega$ resistors (which have a total resistance of $15\text{-}\Omega$). B

$$5. \frac{1}{6.7} + \frac{1}{6.7} + \frac{1}{6.7} + \frac{1}{6.7} = \frac{1}{R}$$

$$\frac{4}{6.7} = \frac{1}{R}$$

$$R = \frac{6.7}{4} = \boxed{1.68\text{-}\Omega}$$

6. $q = 1.38 \times 10^{-6}\text{C}$
 $t = 5.72\text{s}$
 $I = ?$

$$I = \frac{q}{t}$$

$$I = \frac{1.38 \times 10^{-6}}{5.72} = \boxed{2.41 \times 10^{-7}\text{A}}$$


7. $R = 205\text{-}\Omega$
 $V = 120\text{V}$
 $I = ?$

$$V = IR$$
$$120 = I(205)$$
$$I = \frac{120}{205}$$

$$\boxed{I = 0.585\text{A}}$$

8. The same, because the current along one path is constant. The battery is on one path, so the current would be the same.

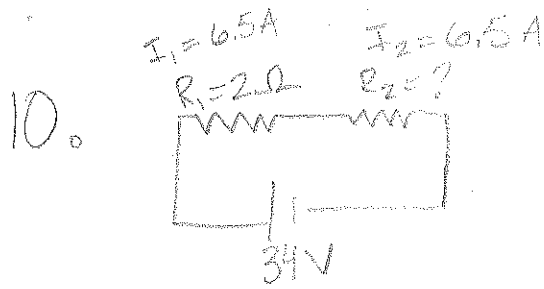9. Parallel because when one goes out, the rest stay on.



we need ΔV_2 , to find R_2
 $\Delta V_1 + \Delta V_2 = 34V$

$$\Delta V_1 = I_1 \cdot R_1$$

$$\Delta V_1 = (6.5)(2) = 13V$$

$$\Delta V_2 = 34 - 13 = 21V$$

$$\Delta V_2 = I_2 \cdot R_2$$

$$\frac{21 = 6.5 R_2}{6.5}$$

$$R_2 = 3.23 \Omega$$

11. $\Delta V = 9.2 \Omega$
 $I = 4.6 A$
 $R = ?$

a) $\Delta V = IR$
 $9.2 = 4.6 R$
 $\frac{9.2}{4.6}$
 $R = 2 \Omega$

b) parallel:

$$\frac{1}{2} + \frac{1}{2} = \frac{1}{R}$$

$$\frac{2}{2} = \frac{1}{R}$$

$$R = 1 \Omega$$

12. $\frac{1}{25} + \frac{1}{25} + \frac{1}{25} + \frac{1}{25} = \frac{1}{R_1}$
 $\frac{4}{25} = \frac{1}{R_1}$ $R_1 = \frac{25}{4} = 6.25 \Omega$

$$\frac{1}{10} + \frac{1}{10} + \frac{1}{10} + \frac{1}{10} = \frac{1}{R_2}$$


$$\frac{4}{10} = \frac{1}{R_2}$$

$$R_2 = \frac{10}{4} = 2.5 \Omega$$

$$R = 6.25 + 2.5$$

$$R = 8.75 \Omega$$

B.

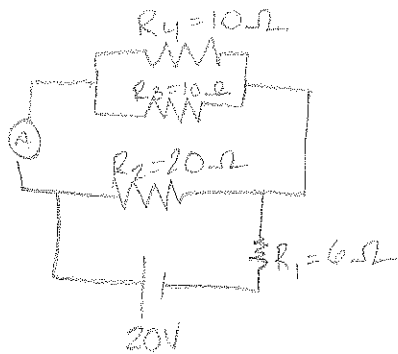

Step 3: Find current thru ammeter.

$$I = I_T - I_2$$

$$I = 2 - .4 = 1.6 \text{ A}$$

step 1: Find total current

1a) find total resistance

$$\frac{1}{10} + \frac{1}{10} + \frac{1}{20} = \frac{1}{R_{234}}$$

$$R_T = R_{234} + R_1 = 4\Omega + 6\Omega$$

$$R_T = 10\Omega$$

$$\frac{5}{20} = \frac{1}{R_{234}}$$

$$R_{234} = 20/5 = 4\Omega$$

1b) use Ohm's law to find total current

$$V = IR$$

$$\frac{20}{10} = I(10) \quad I_T = 2 \text{ A}$$

step 2: Use Kirchoff's Law ($\Delta V = 0$ on a closed loop) to find current through R_2 .

The current we want will be $I_T - I_2$

- On the path w/ R_2 there are two resistors $R_1 + R_2$, they will each take some voltage.

- R_1 has the full current flowing through it, so we can find its ΔV .

$$\Delta V = I_1 R_1 = 2(6) = 12 \text{ V}$$

- $\Delta V = 0 \therefore 20 - 12 - V_2 = 0$ Δ finding ΔV of Resistor 2.

$$V_2 = 8 \text{ V}$$

- Now we can find I_2

$$V_2 = I_2 R_2 \quad 8 = I(20)$$

$$I_2 = 8/20 = .4 \text{ A}$$