
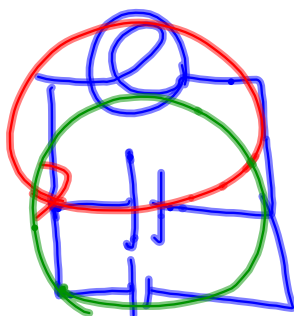


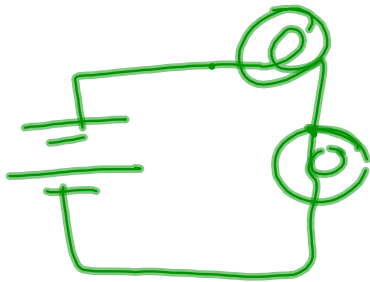
- light bulb got brighter
- doubled voltage, increased current



- same brightness as 1 battery
- But more current



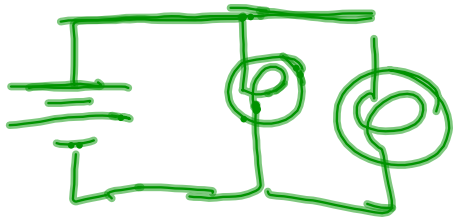* if one goes out
both go out
* about the same brightness
as a single bulb.



* much brighter



Parallel Resistors lower resistance of the circuit.

Equivalent Resistance:

$$R_s = R_1 + R_2 + R_3 + \dots$$

→ series
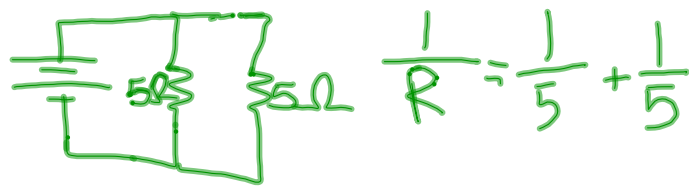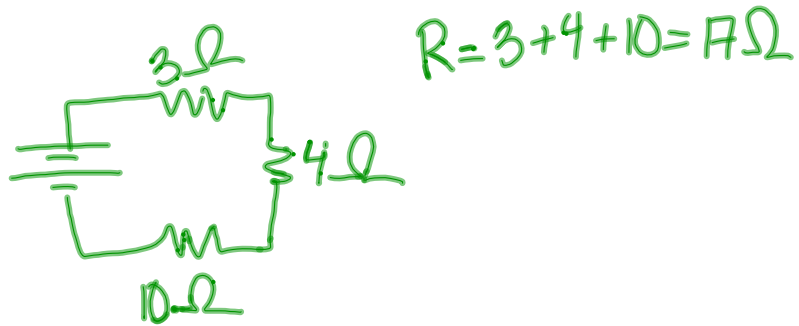
$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$$



$$R \cdot 5 \cdot \left(\frac{1}{R} = \frac{2}{5} \right) R \cdot 5$$

$$R = \frac{5}{2}$$

$$\frac{5 = 2R}{2} \\ R = \frac{5}{2}$$






$$\frac{1}{R_T} = \frac{1}{6} + \frac{1}{4} + \frac{1}{10}$$

$$\frac{1}{R_T} = \frac{.51666}{1}$$

$$R_T = \frac{1}{.51666}$$

$$R_T = 1.9\Omega$$

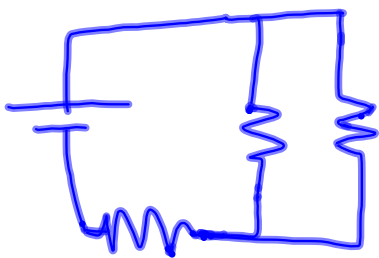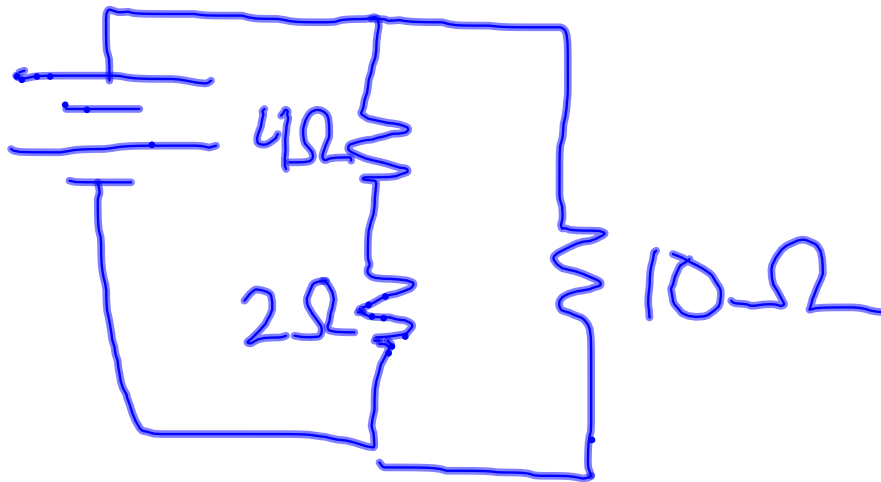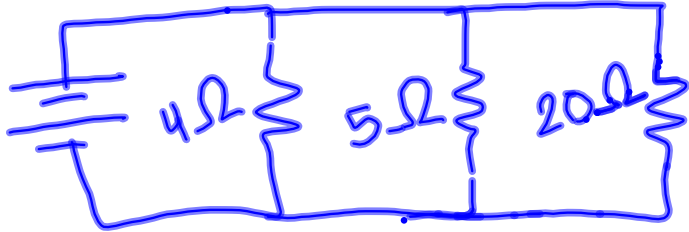

$R=2$

\Downarrow - Davis