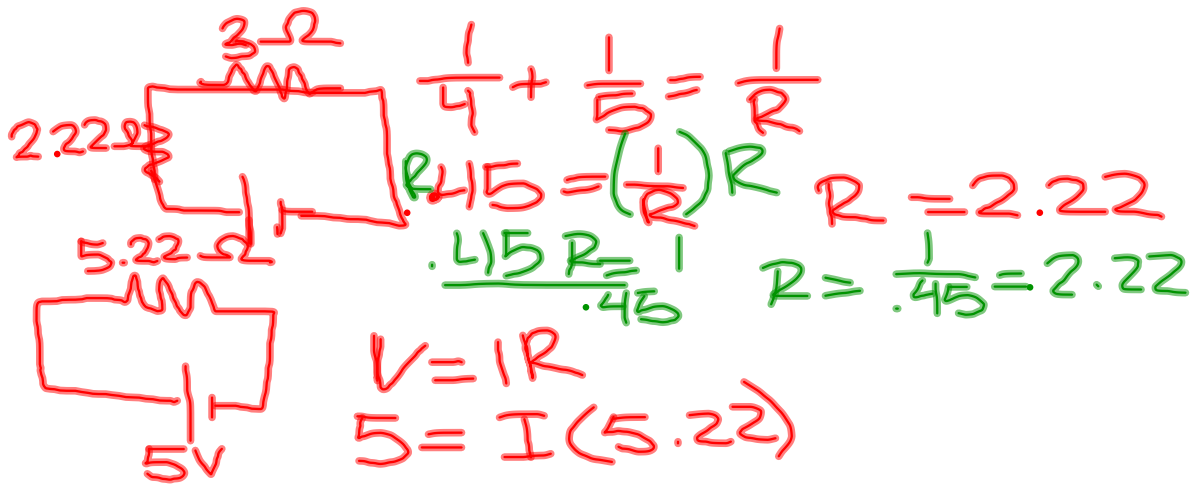
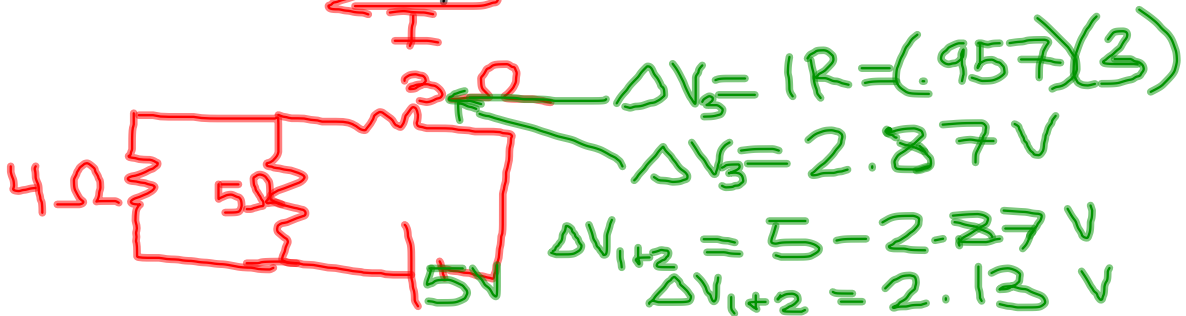


$2.13V = I_1(5\Omega)$   
 $I_1 = 0.43$   
 $2.13V = I_2(4\Omega)$   
 $I_2 = .53$



$I = .957 A$